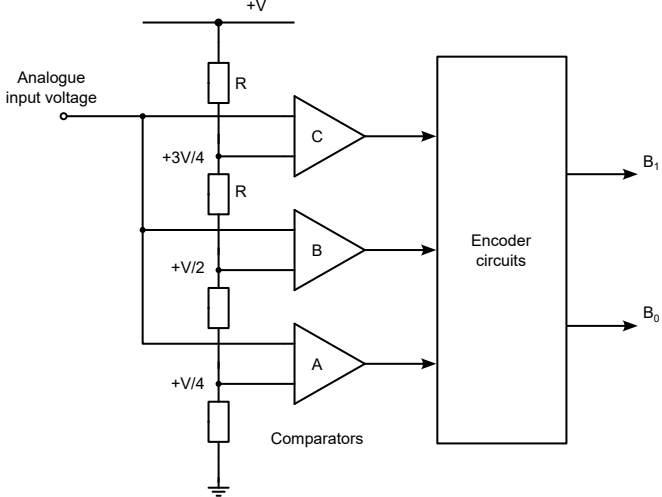




Analogue Input Voltage	Comparator Outputs			Binary Outputs	
	A	B	C	B_0	B_1
0 to $V/4$	0	0	0	0	0
$V/4$ to $V/2$	1	0	0	0	1
$V/2$ to $3V/4$	1	1	0	1	0
$3V/4$ to V	1	1	1	1	1