

14 marks

The diagram shows a rectangular magnetic core with an outer width of 120 and an outer height of 135. The inner width is 120 - 2*30 = 60, and the inner height is 135 - 2*30 = 75. The air gap is 30. The coil has 3 turns. The magnetic field B is indicated by a dashed line.

Figure 1 consists of two graphs, (1) and (2), showing the relationship between magnetic induction B (in T) and magnetic field strength H (in A/cm).


Graph (1) shows a single curve (1) starting at the origin (0,0) and increasing monotonically, reaching approximately 1.2 T at $H = 4$ A/cm.

Graph (2) shows two curves, (1) and (2), both starting at the origin (0,0) and increasing monotonically. Curve (1) reaches approximately 2.2 T at $H = 400$ A/cm, while curve (2) reaches approximately 1.8 T at $H = 400$ A/cm.


1.1. Calculate the magnetic flux ϕ_δ in the air gap.

[illegible]


- 1.2. How big is the magnetic flux density B_{Fe} in the iron core at the dotted line in Fig. 1.1? Neglect the leakage flux.

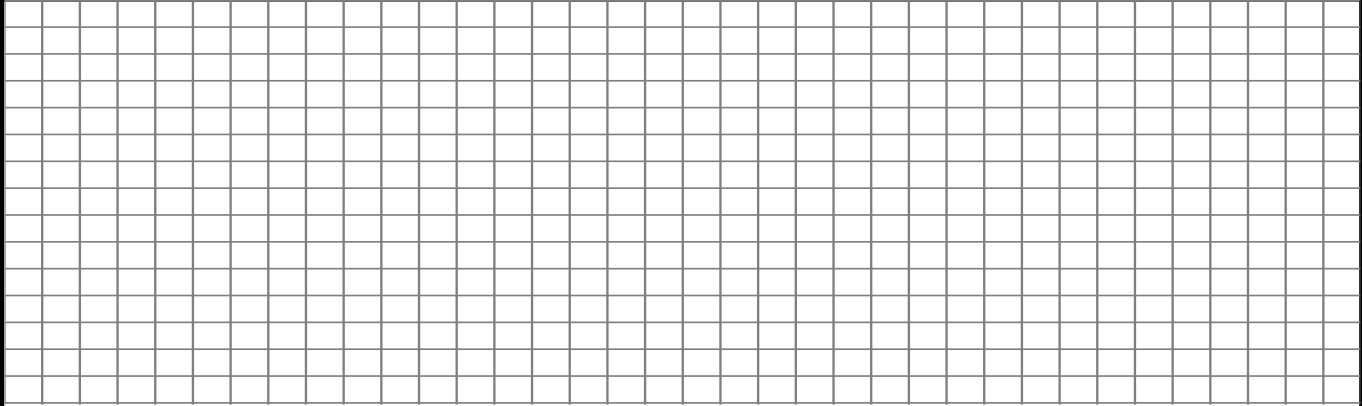

Final solution: _____ (____ / 2)

- 1.3. What is the value of the permeability μ and the magnetic field strengths H_{δ} and H_{Fe} in the air gap and in the iron for the given operating point?

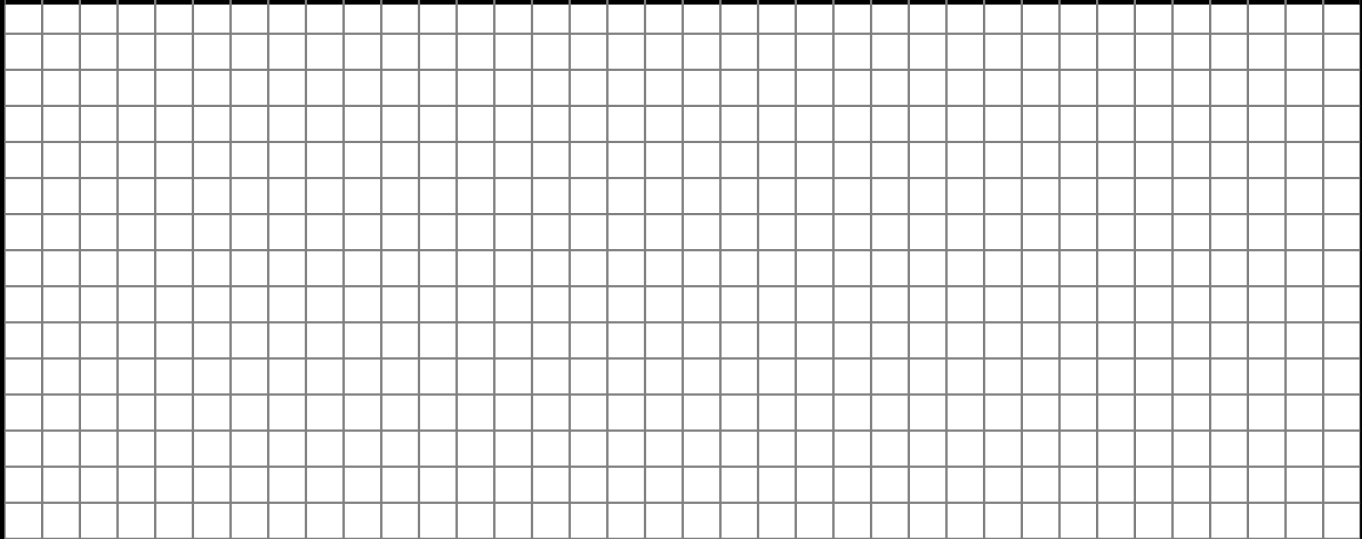

Final solution: _____ (____ / 4)

- 1.4. What is the required magnetomotive force $\theta = N \cdot I$ in the excitation coil to excite the flux density $B_{\delta} = 1.8 \text{ T}$?

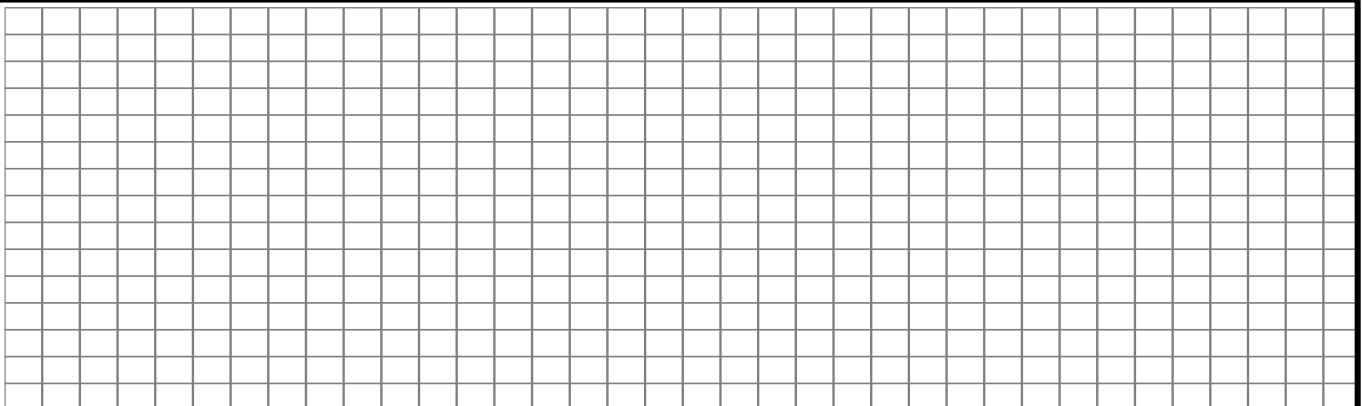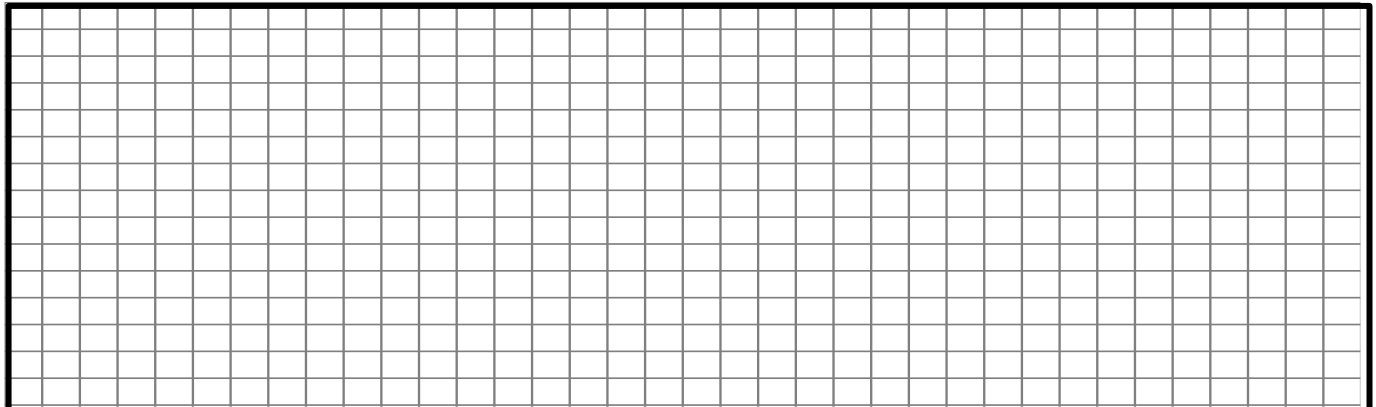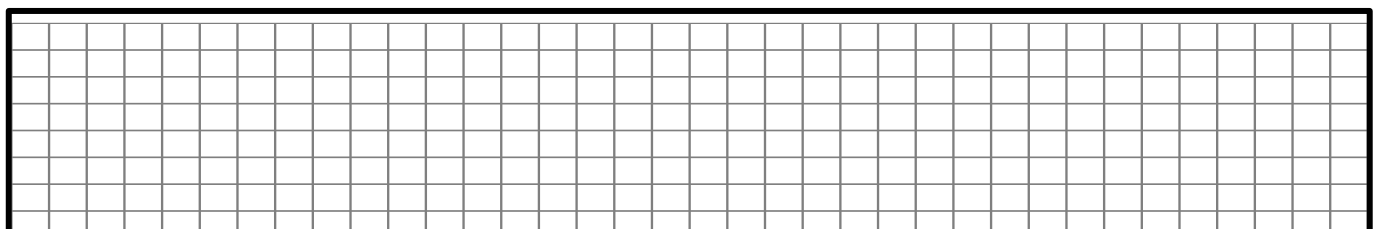
--


Final solution: _____ (____ / 5)

1.5. What is the required current I if the coil has $N = 500$ turns?

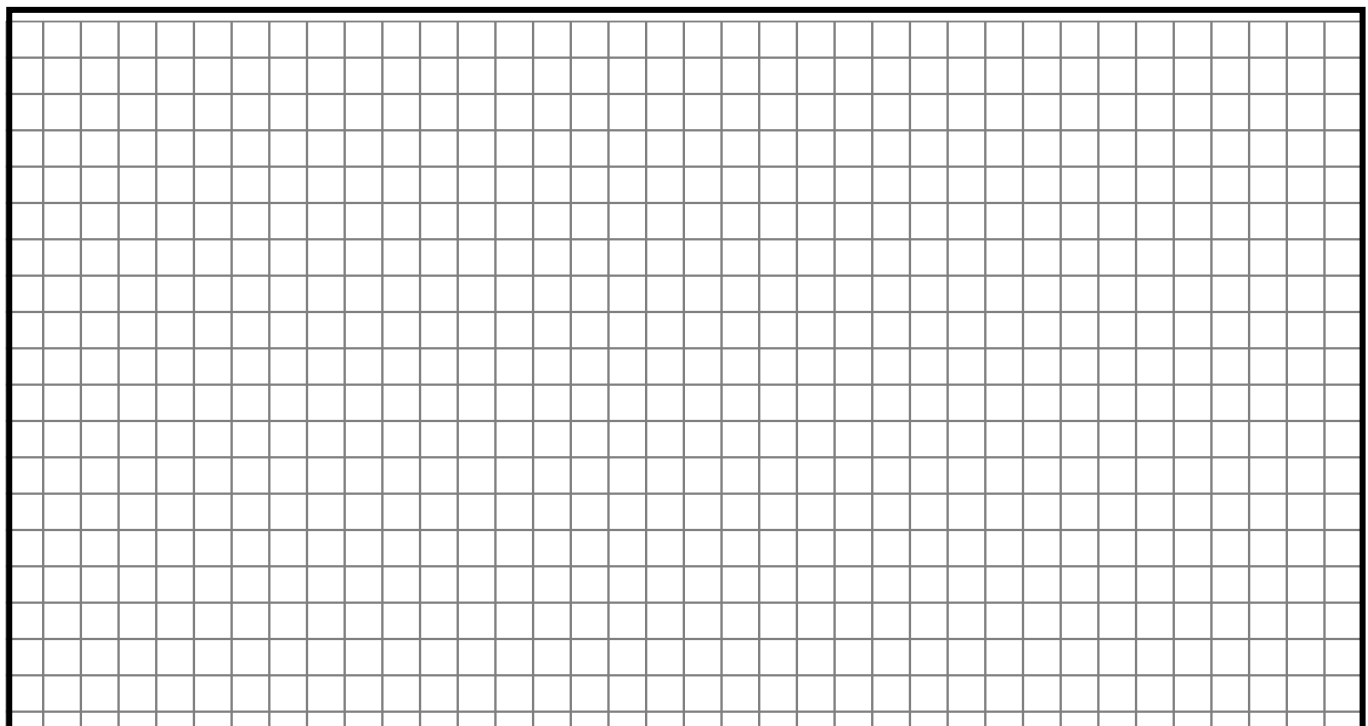

Final solution: _____ (____ / 1)

Question 2: Three-phase transformer

16 marks

A three-phase step-down transformer is connected to 6600 V mains and takes a current of 24 A. The ratio of turns per phase is 12. Assume ideal conditions, no losses. Calculate the (i) secondary line voltage, (ii) line current and (iii) output power, for the following connections:

2.1. Δ - Δ (Delta-Delta)


Final solutions: _____ (____ / 4)

Final solutions: _____ (_____/4)

Final solutions: _____ (_____/4)

2.4.Star-Δ

Final solutions: _____
(____/4)

Question 3: Four quadrants of machine operation

4 marks

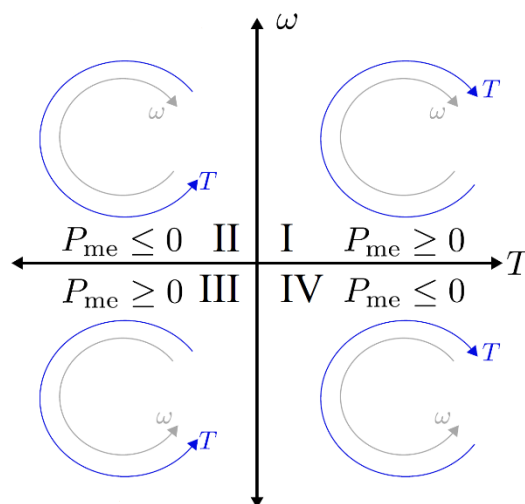


Fig. 3: Diagram for Question 3

Fig. 3 shows the operating modes of an electrical machine in four quadrants. Define the operating modes of each quadrant:

3.1. First quadrant	
3.2. Second quadrant	


3.3. Third quadrant	
3.4. Fourth quadrant	

Question 4: Power Semiconductor devices

4 marks

The following plots show the ideal characteristics of either of the following devices:

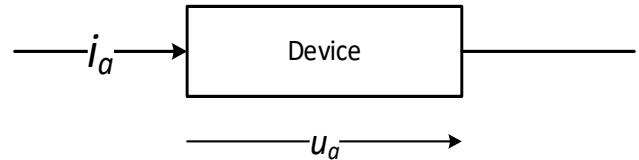
- Diode
- Thyristor
- Insulated Gate Bipolar Transistor
- Power Metal Oxide Semiconductor Field Effect Transistor (MOSFET)



The current flowing through the component is i_a and the voltage drop across the component is u_a . Enter the name of the associated part under each diagram:

(____/4)	

For the converter topology given in Fig. 6, draw the waveforms considering the control pulses defined in the plot below for T . Assume operation in continuous conduction mode. The amplitude of each parameter is already mentioned in the schematic. There is no need to compute values; just waveforms are expected.

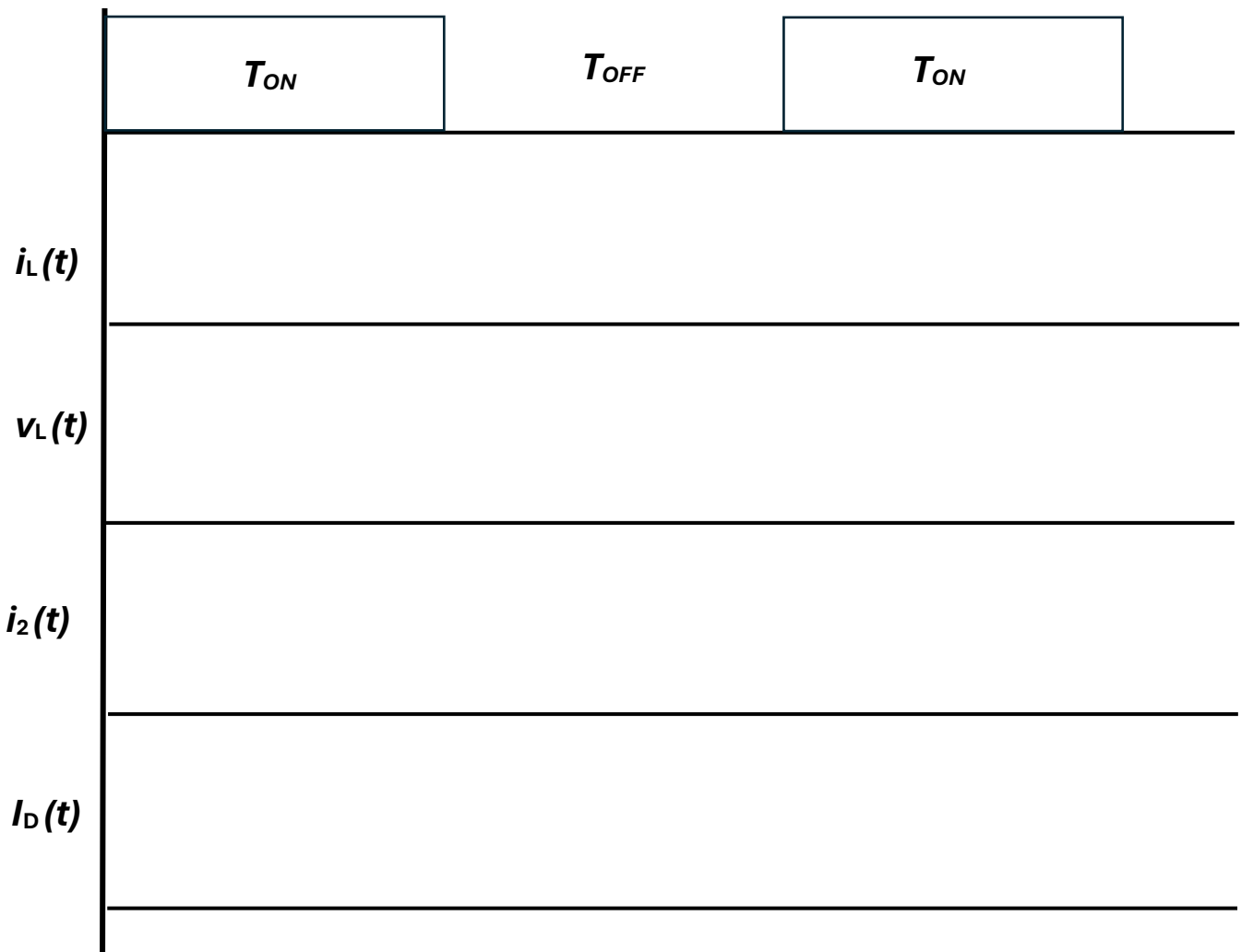

Question 7: Isolated power converter analysis

4 marks


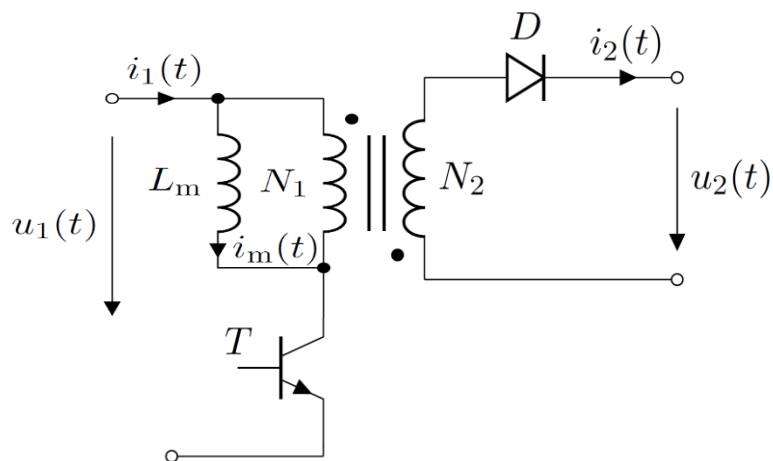


Fig. 6: Schematic of a buck/boost converter

For the converter topology given in Fig. 7, draw the waveforms considering the control pulses defined in the plot below for T . Assume operation in continuous conduction mode. The amplitude of each parameter is already mentioned in the schematic. There is no need to compute values; just waveforms are expected.

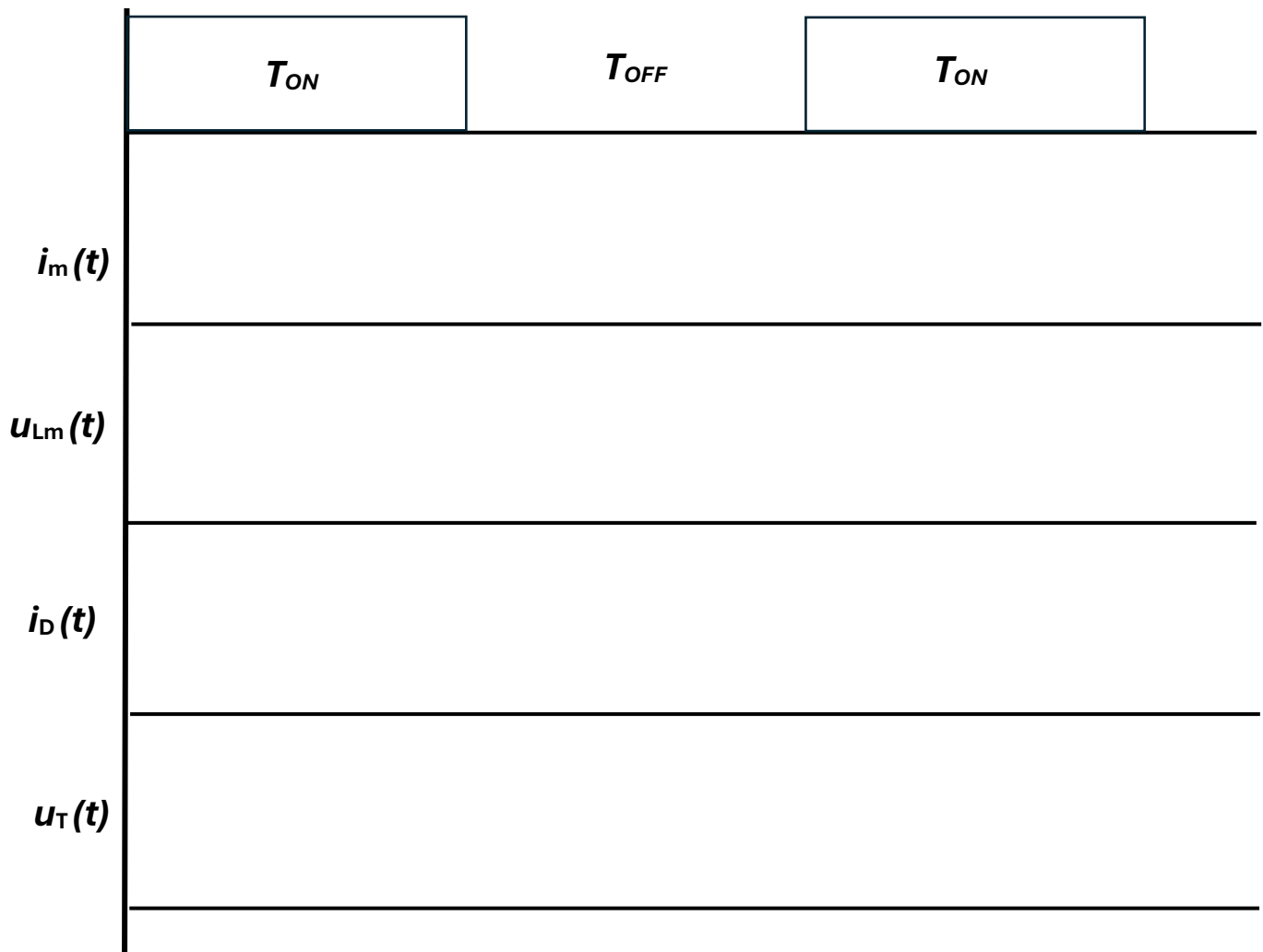

Question 8: Isolated converter numerical

10 marks

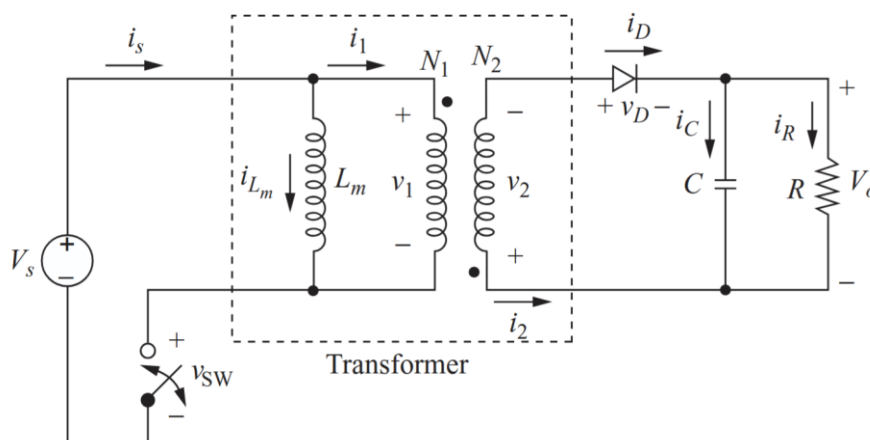


Fig. 7. Schematic of the converter under investigation


The above circuit has the following parameters:

7.1. The required duty ratio- D

Final solution: _____	(____ / 2)
-----------------------	--------------

Final solution: _____
(_____/6)

7.3. The output voltage ripple

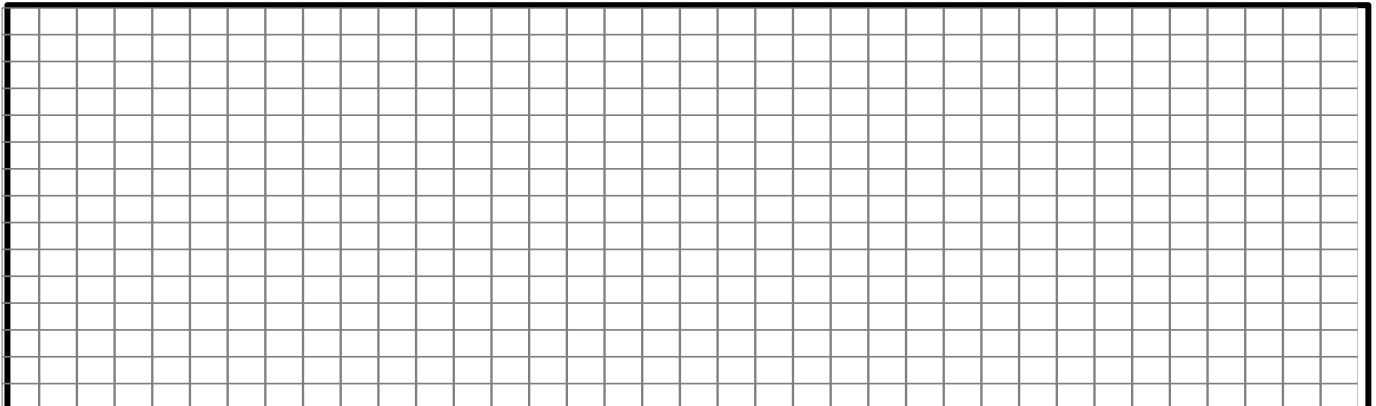

Final solution: _____

(____ / 2)